


Task -1

DAY #6

Team- 2

Ankush, Kush, Kushagra, Ajay Sharma, Ajay Prakash, Shrishti, Shashank, Shubham Chaurasia

CMOS Layout of 2-INPUT AND Gate

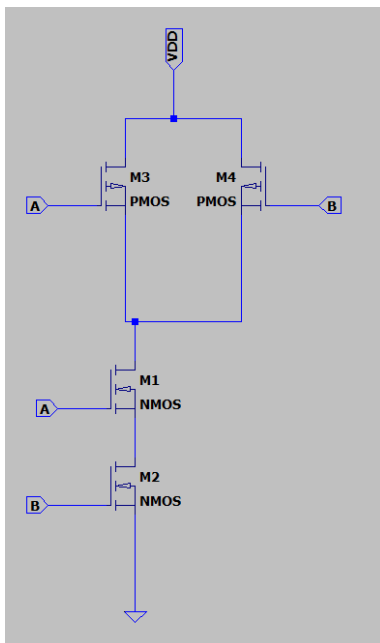

Day #6

Task-1

Cmos 2-input AND layout

Ankush, Kush, Kushagra, Ajay Sharma, Ajay Prakash, Shrishti, Shashank, Shubham Chaurasia

