


Task -2

DAY #6

Team- 2

Ankush, Kush, Kushagra, Ajay Sharma, Ajay Prakash, Shrishti, Shashank, Shubham Chaurasia

CMOS Layout of expression : $A + B.C$

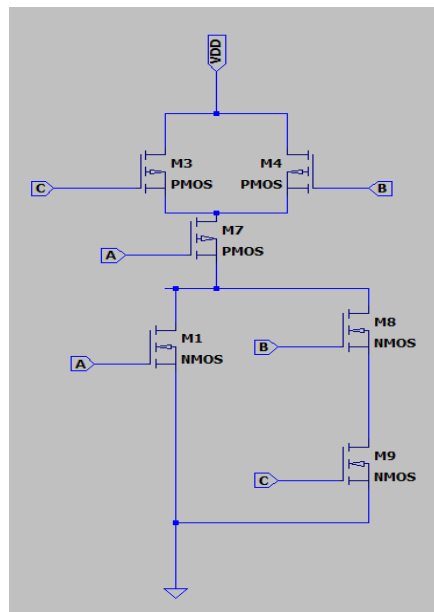

Day #6

Task -2

Team- 2

Ankush, Kush, Kushagra,
Ajay Sharma, Ajay Prakash,
Shrishti, Shashank,
Shubham Chaurasia

